

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5352]-535

S.E. (E&TC/Electronics) (I Sem.) EXAMINATION, 2018
DIGITAL ELECTRONICS
(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Assume suitable data, if necessary.

Q 1 a Design a full adder using two half adders. 4 M

b Minimize the following expression using k-map and
implement using logic gates 4 M
 $Y = \sum m(4, 5, 6, 7, 12, 13, 14, 15)$

c State the types of shift register and explain any one of them 4 M

Q 2 a Design 3 bit synchronous counter using Delay flip flop(D-FF) 6 M

B Design 4:1 MUX using 2:1 MUX 6 M

Q 3 a Explain Mealy and Moore circuits with diagram? 6 M

b Draw and explain operation of Tri-state TTL inverter? 6 M

Q 4 a Explain the terms related to ASM chart. 6 M

I. state box

II. Decision box

III. conditional box

b Draw and explain the working of 2 input CMOS Inverter 6 M

P.T.O.

- Q 5 a Implement the following functions using PLA 6 M
- $F1 = \sum m(0, 2, 4, 6)$
- $F2 = \sum m(2, 3, 6, 7)$
- b Explain the characteristics of DRAM. 4M
- c State various types of ROMS and their applications. 3M
- Q 6 a Draw the internal organization of asynchronous SRAM 6 M
- b Explain the general architecture of CPLD 4M
- c Explain the difference between PLA and PAL 3M
- Q 7 a Draw and explain block diagram of microcontroller 6 M
- b Explain stack operation and stack pointer register of 8051 4M
- c What are the different modes of timer of 8051? 3M
- Q 8 a Explain 8051 port structure with neat diagram 6 M
- b Explain the use of DPTR 4M
- c State salient features of 8051 microcontroller 3M